



National University
of Computer and Emerging Sciences
Chiniot-Faisalabad Campus



NS 1001 - Applied Physics

Q1:- Given :

$$q = 70 \text{ pC} = 70 \times 10^{-12} \text{ C}$$

$$V = 20 \text{ V}$$

Solution:

a) $C = \frac{q}{V}$

$$C = \frac{70 \times 10^{-12}}{20}$$

$$C = 3.5 \times 10^{-12} \text{ F}$$

b) We know that capacitance do not depend on charge. So, the capacitance remain

$$C = 3.5 \times 10^{-12} \text{ F}$$

c) If $q = 200 \times 10^{-12} \text{ C}$

then, $V = \frac{200 \times 10^{-12}}{3.5 \times 10^{-12}}$

$$V = 57 \text{ V}$$

Q4:- Given:

a radius = $38 \times 10^{-3} \text{ m}$

b radius = $40 \times 10^{-3} \text{ m}$

Sol :-

a) $C = 4\pi\epsilon_0 \frac{ab}{b-a}$

$$= 1.11 \times 10^{-10} \times \frac{(38 \times 10^{-3})(40 \times 10^{-3})}{(40 \times 10^{-3}) - (38 \times 10^{-3})}$$

$$C = 8.436 \times 10^{-11} \text{ F}$$

$$b) C = \frac{A\epsilon_0}{d} \Rightarrow A = \frac{Cd}{\epsilon_0}$$

$$= \frac{8.436 \times 10^{-11} \times (40-38) \times 10^{-3}}{8.85 \times 10^{-12}}$$

$$\boxed{A = 191 \text{ cm}^2}$$

Q7: Given:

$$d_s = 10^{-12} \text{ m}$$

$$V_s = 20 \text{ V}$$

Solution:

$$q = Ne \text{ — i)}$$

$$N = nAd \text{ put in i)} \Rightarrow q = nAde \text{ — ii)}$$

$$q = eV \text{ — iii)}$$

Comparing ii) and iii)

$$eV = nAde \Rightarrow C/A = \frac{nde}{V}$$

$$= \frac{8.49 \times 10^{28} \times 10^{-12} \times 1.6 \times 10^{-19}}{20}$$

$$\boxed{C/A = 6.79 \times 10^{-4} \text{ F/m}^2}$$

Q11: Given:

$$C_1 = 10 \mu F$$

$$C_2 = 5 \mu F$$

$$C_3 = 4 \mu F$$


Solution:

$$C_{12} = C_1 + C_2 = (10 + 5) \mu F = 15 \mu F$$

$$\begin{aligned} \frac{1}{C_{eq}} &= \frac{1}{C_{12}} + \frac{1}{C_3} \\ &= \frac{1}{15} + \frac{1}{4} = \frac{15+4}{60} \end{aligned}$$

$$\frac{1}{C_{eq}} = \frac{19}{60} \Rightarrow C_{eq} = \frac{60}{19}$$

$$C_{eq} = 3.1578 \mu F$$

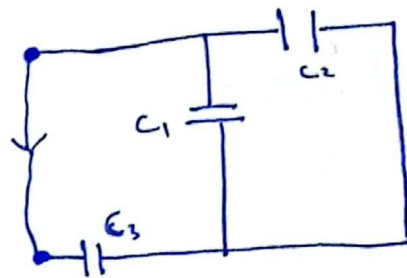


Q14: Given:

$$V = 10V$$

$$C = 10 \mu F \text{ for all capacitors}$$

Solution:

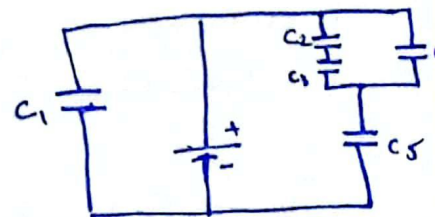

$$a) q_1 = C_1 V = 10 \times 10^{-6} \times 10 = 10^{-4} C$$

$$b) \boxed{q_1 = 10^{-4} C}$$
$$C_{23} = \frac{C_2 C_3}{C_2 + C_3} = \frac{100}{20} = 5 \mu F$$

$$C_{234} = C_{23} + C_4 = 5 \mu F + 10 \mu F = 15 \mu F$$

$$C_{2345} = \frac{C_{234} C_5}{C_{234} + C_5} = 6 \mu F$$

$$C_{eq} = C_1 + C_{2345} = 10 \mu F + 6 \mu F = 16 \mu F$$

$$q_{2345} = C_{2345} V = 6 \mu F \cdot 10 V = 60 \mu C$$

$$q_2 = C_{23} V_{23} = 5 \times \frac{60}{15} = 5 \times 4$$

$$q_2 = 20 \mu C$$

$$\begin{aligned} V_{23} &= \frac{Q_{234}}{C_{234}} \\ &= \frac{60}{15} \\ &= 4 \end{aligned}$$

Q27: Given:

$$C_1 = 1 \mu F, C_2 = 2 \mu F, C_3 = 3 \mu F, C_4 = 4 \mu F$$

Solution:

$$a) q_1 = C_{13} V = \frac{C_1 C_3}{C_1 + C_3} V = \frac{1 \cdot 3}{1+3} \times 12 = \frac{3}{4} \times 12 = 9 \mu C$$

$$b) q_2 = C_{24} V = \frac{C_2 C_4}{C_2 + C_4} \times 12 = \frac{8}{6} \times 12 = 16 \mu C$$

$$c) q_3 = q_1 = 9 \mu C$$

$$d) q_4 = q_2 = 16 \mu C$$

$$e) V_1 = \frac{C_3 + C_4}{C_1 + C_2 + C_3 + C_4} V = \frac{3+4}{1+2+3+4} \times 12 = \frac{7}{10} \times 12 = 8.4 V$$

$$q_1 = C_1 V_1 = 1 \times 8.4 = 8.4 \mu C$$

$$f) q_2 = C_2 V_1 = 2 \times 8.4 = 16.8 \mu C$$

$$g) q_3 = C_3 (12 - V_1) = 3 \times (12 - 8.4) = 10.8 \mu C$$

$$h) q_4 = C_4 (12 - V_1) = 4 \times (12 - 8.4) = 14.4 \mu C$$