

Department of Electrical Engineering
*National University of Computer and
Emerging Sciences,
Chiniot-Faisalabad Campus*



**EL-1005: DIGITAL LOGIC DESIGN
LABORATORY MANUAL
FALL 2022**

Name: _____

Roll No: _____

Section: _____

Lab Manual of 'Digital Logic Design'

➤ Created by: Mr. M. Umair Akram Butt
Mr. Soban Ahmad
Date: January, 2019

➤ Revised by: Mr. M. Umair Akram Butt
Mr. Soban Ahmad
Mr. M. Arslan
Date: January, 2020

➤ Last Updated by: Mr. Mujahid Hussain
Mr. Faizan Ahmad

Date: August, 2021

Table of Contents

Sr. No.	Description	Page No.
1	List of Equipment	4
2	List of Experiments	5
3	Introduction to Trainer Board and Logic Probe	6
4	Introduction to Integrated Circuit (IC's)	12
5	Boolean Expression Implementation	19
6	Universal Gates NAND/NOR Implementation	22
7	Half Adder and Subtractor using Logic Gates	25
8	Boolean Expression Simplification with K Map	27
9	Two Bit Magnitude Comparator	30
10	Encoder & Decoder	32
11	Multiplexer and De-multiplexer	36
12	7 segment Display & sequential Circuits	40
13	Universal Shift Register	45
14	Counters	48
15	Appendix A: Lab Evaluation Criteria	54
16	Appendix B: Safety around Electricity	55

List of Equipment

Sr. No.	Description
1	Digital Logic Design Trainer Board
2	Bread Board
3	74XX Logic Gate ICs
4	Logic Probe
5	2N2222 Transistors
6	Jumper Wires
7	Wire Cutters

List of Experiments

Sr. #	Title of Experiment
01	Introduction to Trainer Board and Logic Probe
02	Introduction to Integrated Circuit (IC's)
03	Boolean Expression Implementation
04	Boolean Expression Simplification with K Map
05	Universal Gates NAND/NOR Implementation
06	Half Adder and Subtractor using Logic Gates
07	Two Bit Magnitude Comparator
08	Encoder & Decoder
09	Multiplexer and De-multiplexer
10	7 segment Display & sequential Circuits
11	Universal Shift Register
12	Counters

EXPERIMENT 1

Date Perform: _____

Introduction to Trainer Board and Logic Probe

1.1 OBJECTIVE:

- To become familiar with the components of the trainer board used in the digital experiments
- To become familiar with configuration of Bread Board
- To become familiar with the Logic Probe.

1.2 EQUIPMENT:

- Trainer Board
- Bread Board
- Logic Probe

1.3 BACKGROUND:

Trainer Board:

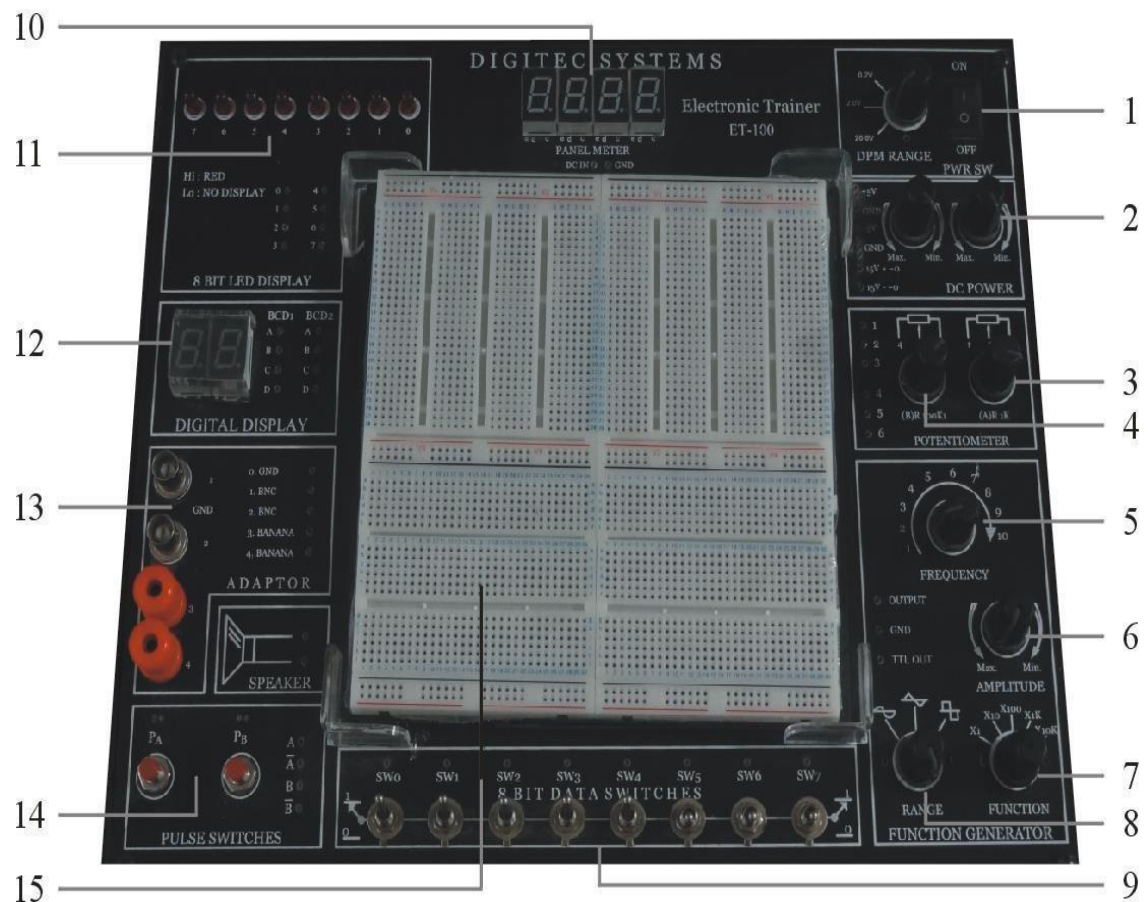


Fig. 1: Trainer Board

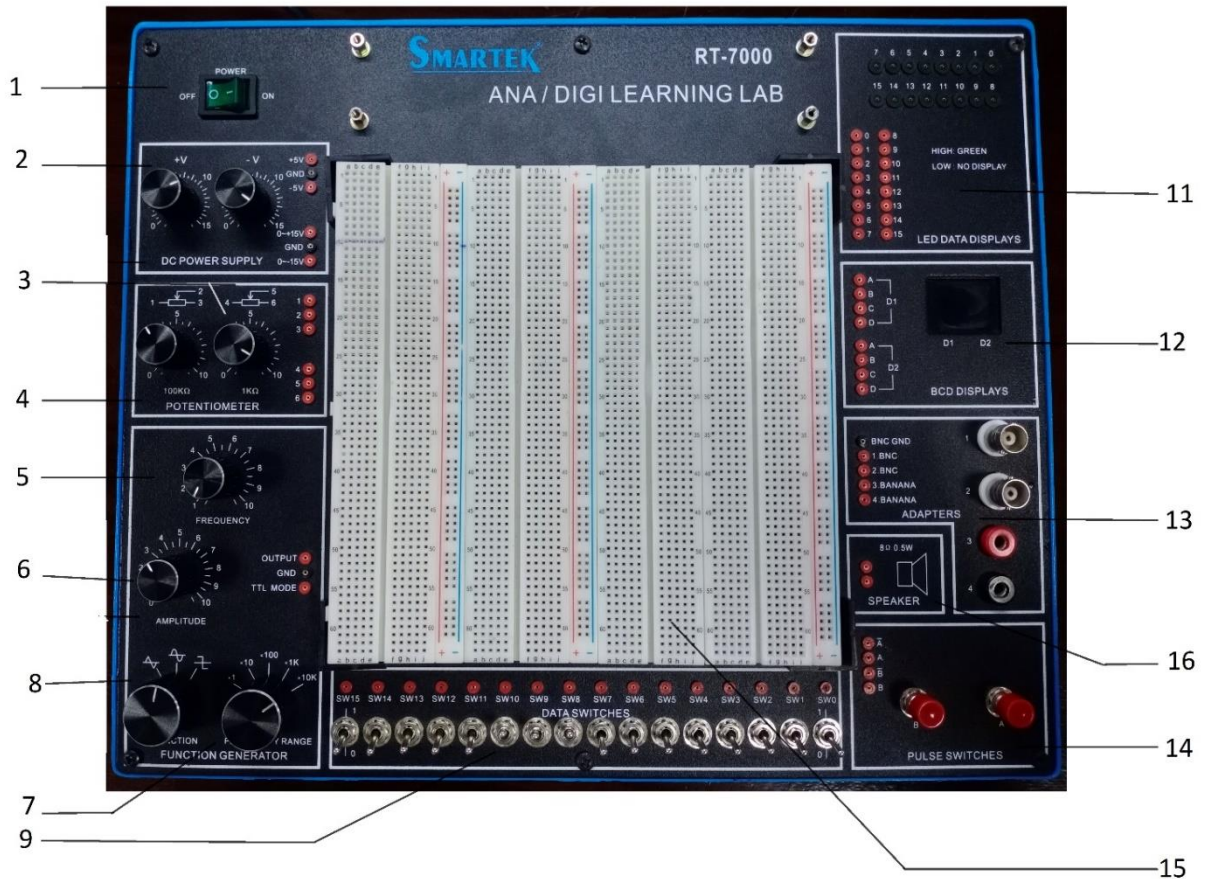


Fig. 1: Trainer Board

1. Power Switches: For On/Off purpose
2. DC power supply: + 5V, -5V (fixed), +15V and - 15V (variable). We will be using +5V in most of our experiments.
3. Potentiometers (VR2 = 100k ohms)
4. Potentiometers (VR2 = 100k ohms)
5. Frequency variable
6. Waveform Amplitude variable
7. Frequency range
8. Frequency selector
9. Data Switches and Status LEDs: 8 switches with logic indicators have been made available on the trainer. Depending on the switch position, a logic high or logic low becomes available on the corresponding output socket from where it can be extended through jumper wire to any digital circuit input. Status LED lights ON with a logic high value and lights OFF with logic low value. The output of switch is output from the trainer and input to the circuit and the output of the circuit is input to the trainer board.
10. Panel voltmeter display
11. LEDs for output. See point 9

12. Two 7-segment displays with BCD input sockets are provided on the trainer board. When binary inputs are provided at the input sockets below each display, the decimal equivalent of the BCD input is displayed. The Lamp Test (! LT) input socket is for checking the display: when this input is low (0) all the segments of the display will glow indicating that the display is functioning properly.
13. Adopter
14. Two pulse switches
15. Removable breadboard for patching digital circuits is provided on the trainer board. As each
16. circuit has to be implemented on the breadboard, so a detail description of the breadboard structure is given below.
17. Speakers

Breadboard:

In general, the breadboard consists of two terminal strips and two bus strips (often broken in the center). Each bus strip has two rows of contacts. Each of the two rows of contacts is a node. That is, each contact along a row on a bus strip is connected together (inside the breadboard). Bus strips are used primarily for power supply connections, but are also used for any node requiring a large number of connections. Each terminal strip has 60 rows and 5 columns of contacts on each side of the center gap. Each row of 5 contacts is a node.

You will build your circuits on the terminal strips by inserting the leads of circuit components into the contact receptacles and making connections with wire. It is a good practice to wire +5V and 0V power supply connections to separate bus strips.

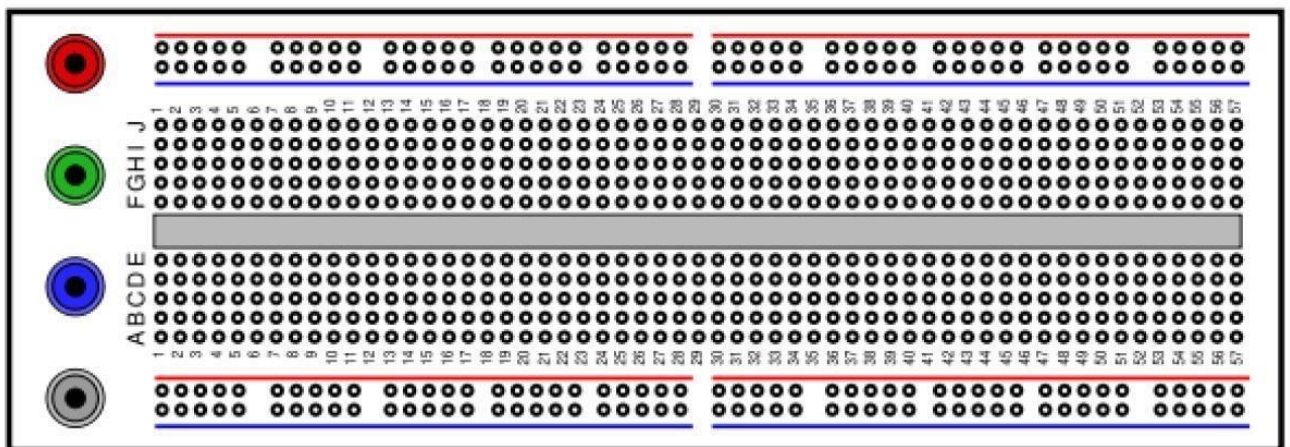


Fig. 1.1: Bread Board

The internal connections are as shown below:

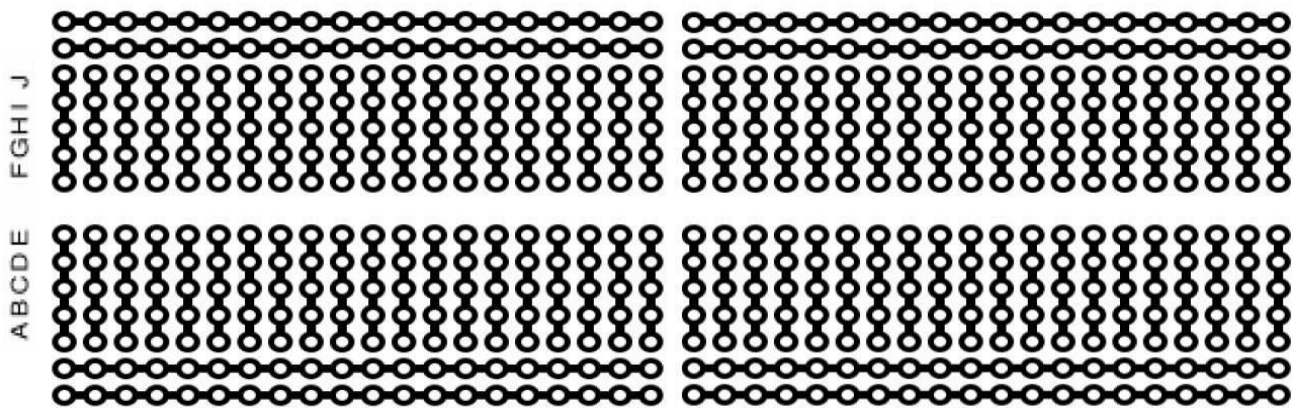


Fig. 1.2: Internal Structure of Bread Board

The points in ABCDE (and FGHIJ) grid are vertically connected as indicated by red circle. So all 5 points on are actually the same point. It makes No difference whether you connect a wire on any one of these points. The next vertical strip is a different point and so on.

It should be noted that upper and lower grids are horizontally connected indicated below. Each grid consists of 4 such separate horizontal strips:

Same Node


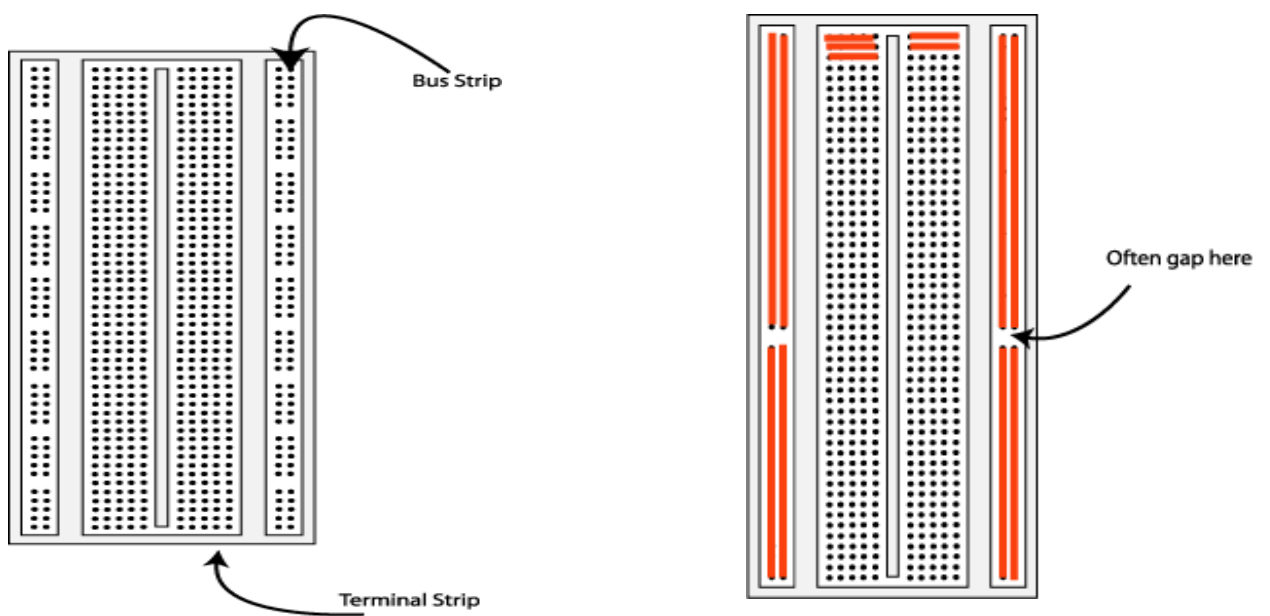


Fig 1.3: Bread Board

In Fig 1.3 the shaded lines indicate connected holes.

Introduction of Logic Probe:

A logic probe can be very handy for troubleshooting and analysis of a digital logic circuit. As compared to a DC voltmeter or an oscilloscope, it needs to distinguish between the states of LOW and HIGH, and so it can be very simple and inexpensive. Its features include two LED indicators: HI (red LED) and LO (green LED).

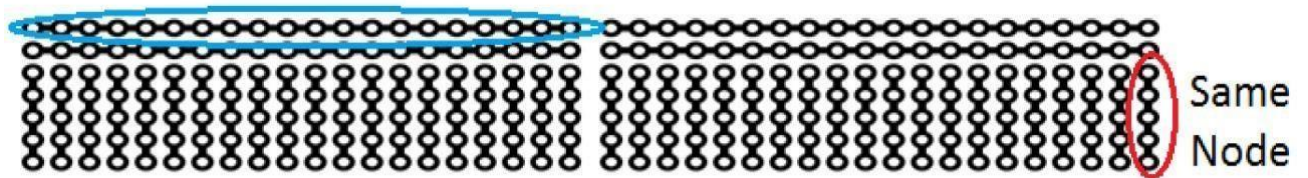

Fig 3.1: Logic Probe

Specifications:

Model:

GLP-1A Logic Probe (50MHz Frequency Displayable)

Operation:

1. Connect the black alligator clip to ground or common of the circuit under test.
2. Connect the red alligator clip to Vcc (4V DC minimum to 18V DC maximum) of the circuit under test.
3. Touch the probe tip to the circuit point under test. The probe's LEDs indicate the logic level or signals present when the circuit node is probed.

The LED response is noted below:

Input signal	LEDs
Logic "1"	HI (Red) ON
Logic "0"	LOW (Green) ON
Bad Logic Level or Open circuit	None
Square Wave < 200kHz	HI and LOW blinking at frequency rate
Square Wave > 200kHz	HI and LOW blinking at frequency rate

Lab Manual of 'Digital Logic Design'

Task 1:

Make connections of logic probe and verify if all the switches are working Properly.

Task 2:

Connect input switches with LEDs and verify their proper operation.

Task 3:

Connect Logic Probe with Pulse switches and observe their operation.

EXPERIMENT 2

Date Perform: _____

Introduction to Integrated Circuit (IC's)**2.1 OBJECTIVE:**

- To become familiar with the different types of Integrated Circuits (ICs), their use and pin number reading.
- Familiarize with different logic families.
- Identify ICs by series number as well as their functional behavior and pin numbers.
- Carry out best wiring practices in digital design.

2.2 EQUIPMENT:

- Trainer Board
- Wires
- Wires Cutter
- IC Clipper
- 7400 quad 2-input NAND gate IC
- 7402 quad 2-input NOR gate IC
- 7404 hex NOT (Inverter) gate IC
- 7408 quad 2-input AND gate IC
- 7432 quad 2-input OR gate IC
- 7486 quad 2-input XOR gate IC
- 4077 quad 2-input XNOR gate IC

2.3 BACKGROUND:

An integrated circuit (IC) is a group of components which may include resistors, low value capacitors and transistors printed on a silicon chip. The individual components of the I.C make up a commonly used circuit. The circuits can range from simple voltage regulators to audio chips for a head unit to a microprocessor for a computer. The chip is packaged in a plastic holder with pins spaced on a 0.1" (2.54mm) grid which will fit the holes on breadboards. Very fine wires inside the package link the chip to the pins.

Pin Numbers:

The pins are numbered anti-clockwise around the IC (chip) starting near the notch or dot. The diagram shows the numbering for 14-pin ICs, but the principle is the same for all sizes. Sometimes the chip manufacturer may denote the first pin by a small indented circle above the first pin of the chip. Remember that you must connect power to the chips to get them to work.

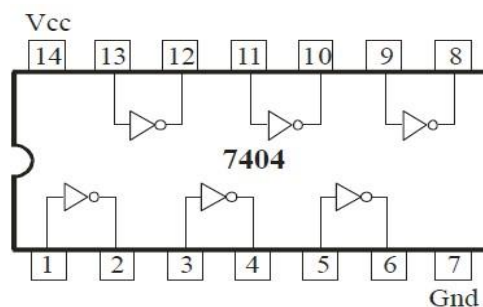


Fig. 1: HEX Inverter

Datasheets:

Datasheets are available for most ICs giving detailed information about their ratings and functions.


Logic ICs (Chips):

Logic chips process digital signals and there are many devices, including logic gates, flip-flops, shift registers, counters and display drivers. They can be split into two groups according to their pin arrangements: the 4000 series and the 74 series which consists of various families such as the 74HC, 74HCT and 74LS. The table below summarizes the important properties of the most popular logic families:

Property	4000 Series	74 Series	74 Series	74 Series
		74HC	74HCT	74LS
Technology	CMOS	High-speed CMOS	High-speed CMOS TTL compatible	TTL Low-power Schottky
Power Supply	3 to 15V	2 to 6V	5V $\pm$ 0.5V	5V $\pm$ 0.25V
Inputs	Very high impedance. Unused inputs must be connected to +Vs or 0V. Inputs cannot be reliably driven by 74LS outputs unless a 'pull-up' resistor is used (see below).		Very high impedance. Unused inputs must be connected to +Vs or 0V. Compatible with 74LS (TTL) outputs.	'Float' high to logic 1 if unconnected. 1mA must be drawn out to hold them at logic 0.
Outputs	Can sink and source about 5mA (10mA with 9V supply), enough to light an LED. To switch larger currents, use a transistor.	Can sink and source about 20mA, enough to light an LED. To switch larger currents use a transistor.	Can sink and source about 20mA, enough to light an LED. To switch larger currents, use a transistor	Can sink up to 16mA (enough to light an LED), but source only about 2mA. To switch larger currents use a transistor.
Fan-out	One output can drive up to 50 CMOS, 74HC or 74HCT inputs, but only one 74LS input.	One output can drive up to 50 CMOS, 74HC or 74HCT inputs, but only 10 74LS inputs.		One output can drive up to 10 74LS inputs or 50 74HCT inputs.
Maximum Frequency	about 1MHz	about 25MHz	about 25MHz	about 35MHz
Power consumption	A few μ W.	A few μ W.	A few μ W.	A few mW

IC Placement on Breadboard

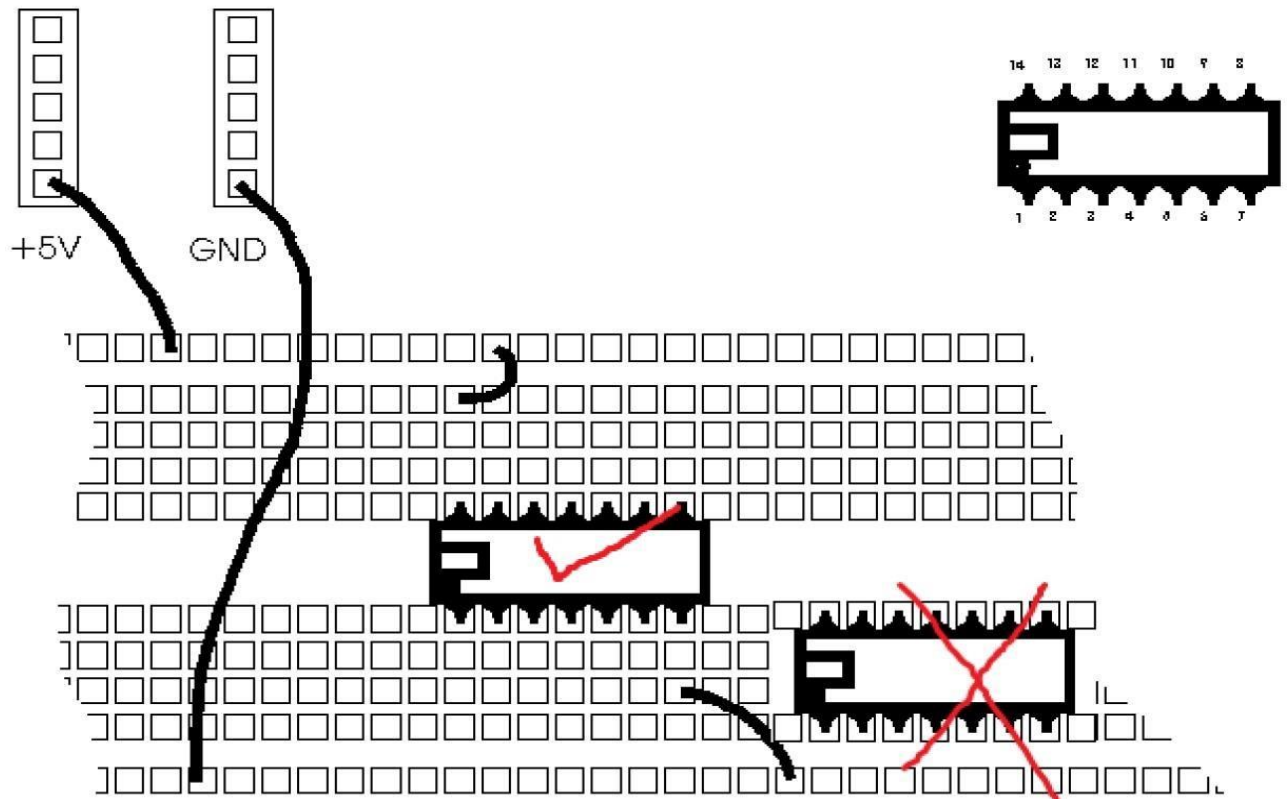A typical 14 pin IC placement on such a bread board is shown below: The upper and lower horizontal strips are normally served for power (+5V) and ground (0V) respectively. But it is not necessary to do so.



Note:

Never place any IC such that its opposite pins are within (connected to) the same Node on the same grid.

Removing a chip from its holder:

If you need to remove a chip it can be gently ejected out of the holder with a small flat-blade screwdriver. Carefully lever up each end by inserting the screwdriver blade between the chip and its holder and gently twisting the screwdriver. Take care to start lifting at both ends before you attempt to remove the chip, otherwise you will bend and possibly break the pins.

3.4 Lab Task:

Throughout these experiments we will use TTL chips to build circuits. The steps for wiring a circuit should be completed in the order described below:

- Turn the power off before you build anything!
- Connect the +5V and ground (GND) leads of the power supply to the power and ground bus strips on your breadboard.

- Plug the chips you will be using into the breadboard. Point all the chips in the same direction with pin 1 at the lower-left corner. (Pin 1 is often identified by a dot or a notch next to it on the chip package)
- Connect +5V and GND pins of each chip to the power and ground bus strips on the bread board.
- Select a connection on your schematic and place a piece of hook-up wire between corresponding pins of the chips on your breadboard. It is better to make the short connections before the longer ones. Mark each connection on your schematic as you go, so as not to try to make the same connection again at a later stage.
- Get one of your group members to check the connections, before you turn the power on.
- If an error is made and is not spotted before you turn the power on. Turn the power off immediately before you begin to rewire the circuit.
- At the end of the laboratory session, collect hook-up wires, chips and all equipment and return them.


Tidy the area that you were working in and leave it in the same condition as it was before you started.

Gates, Their IC Pin Configuration & Truth Tables:

Gate

NOT Gate


Symbol

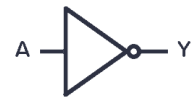

Truth Table

Input (x)	Output (y)
0	
1	


IC Pin Configuration

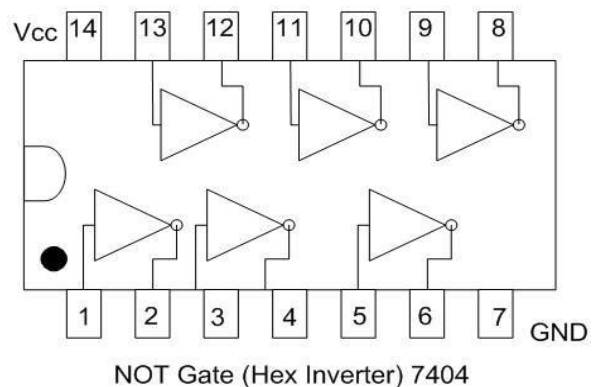

Gate

AND Gate


Symbol

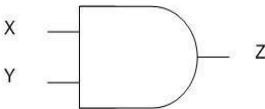

Truth Table

X	Y	Output (Z)
0	0	
0	1	
1	0	
1	1	

IC Pin Configuration

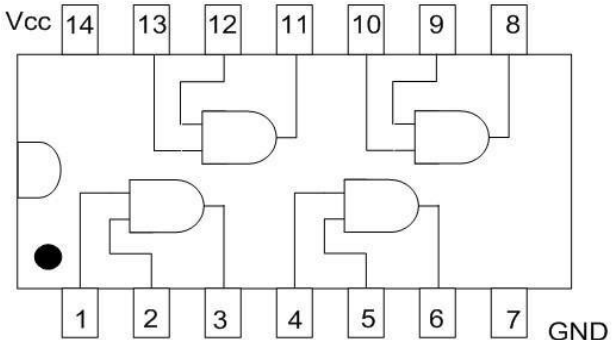


Quad 2-input AND gate 7408

Gate

NAND Gate


Symbol

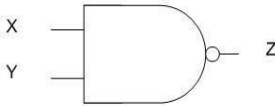

Truth Table

X	Y	Output (Z)
0	0	
0	1	
1	0	
1	1	

IC Pin Configuration

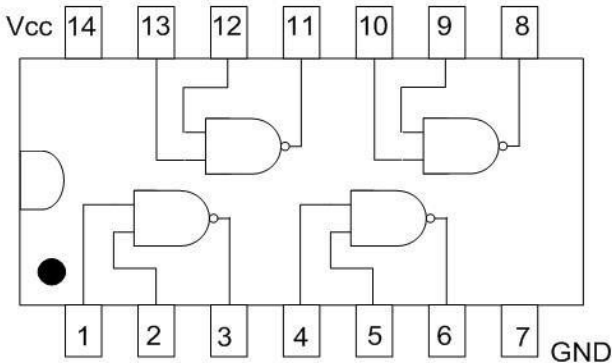


Quad 2-input NAND gate 7400

Gate

OR Gate


Symbol

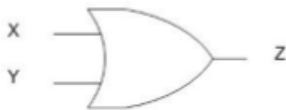

Truth Table

X	Y	Output (Z)
0	0	
0	1	
1	0	
1	1	


IC Pin Configuration

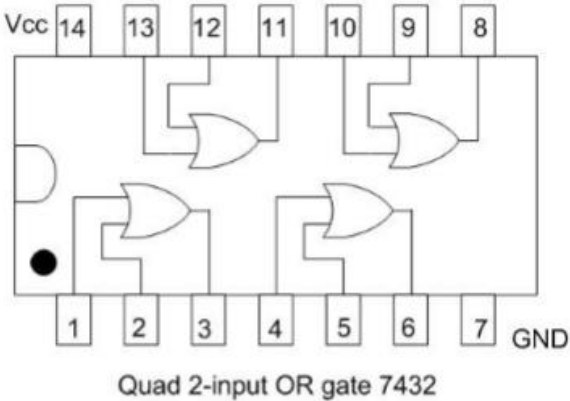

Gate

NOR Gate


Symbol

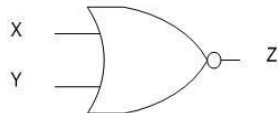

Truth Table

X	Y	Output (Z)
0	0	
0	1	
1	0	
1	1	


IC Pin Configuration

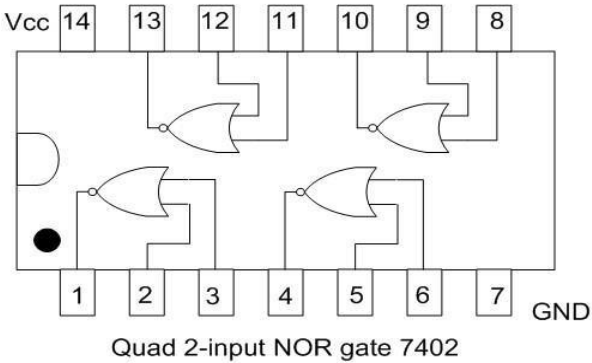

Gate

XOR Gate


Symbol

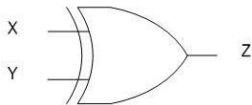

Truth Table

X	Y	Output (Z)
0	0	
0	1	
1	0	
1	1	

IC Pin Configuration

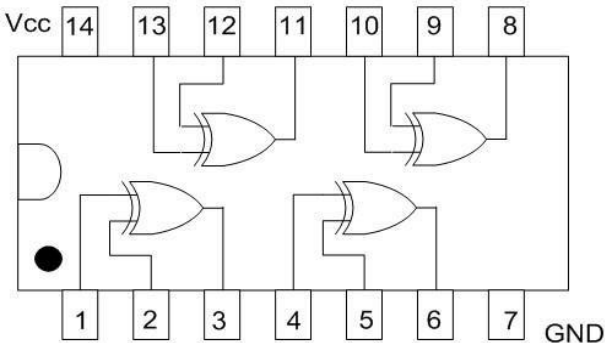


Quad 2-input XOR gate 7486

Gate

XNOR Gate


Symbol

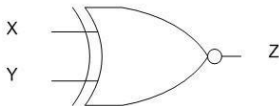

Truth Table

X	Y	Output (Z)
0	0	
0	1	
1	0	
1	1	

IC Pin Configuration

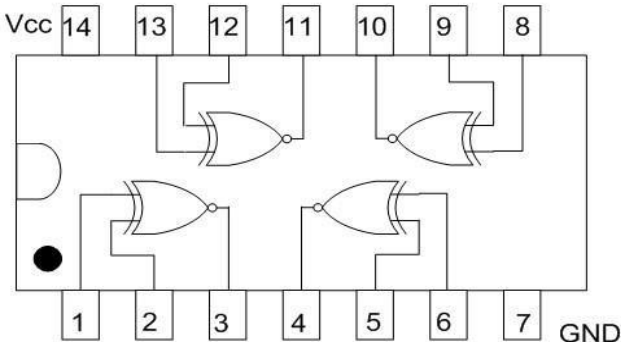

Quad 2-input XNOR gate 4077

EXPERIMENT 3

Date Perform: _____

Boolean Expression Implementation

3.1 OBJECTIVE:


- To become familiar with the realization of Boolean expression through ICs.
- To derive the Boolean Expression from a diagram.
- Learn to draw the equivalent diagram of a given Boolean Expression

3.2 EQUIPMENT:

- Trainer Board
- 7404 hex NOT (Inverter) gate IC ,
- 7432 quad 2-input OR gate IC
- 7408 quad 2-input AND gate IC
- Wires
- Wires Cutter
- IC Clipper

3.3 BACKGROUND:


In the last lab you studied the gates implementation through ICs. The gate operations are represented mathematically as well, as shown in the table below:

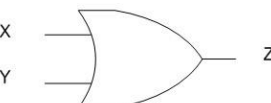Name	Symbol	Boolean Representation
NOT Gate		$Y = \overline{X} \text{ or } X'$
AND Gate		$Z = X \cdot Y$
NAND Gate		$Z = \overline{X \cdot Y} \text{ or } \overline{XY}$
OR Gate		$Z = X + Y$
NOR Gate		$Z = \overline{X + Y}$
XOR Gate		$Z = X \oplus Y$
XNOR Gate		$Z = \overline{X \oplus Y}$

Any digital circuit can be implemented using basic gates and can be represented as a mathematical equation. For example,


$$Z = A + B \cdot C'$$

Will be implemented as follows:

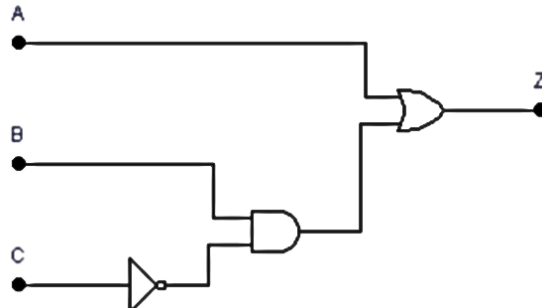

3.4 LAB TASKS:

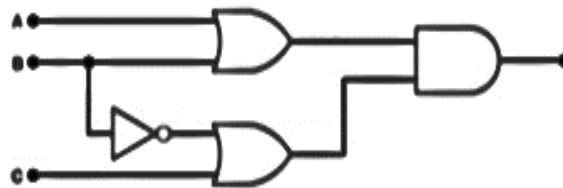- 1) For the given diagram, derive the equivalent Boolean expression, and then draw the truth table and verify it.



F =

A	B	C	F

- 2) For the given function, draw equivalent circuit diagram, draw the truth tables and verify the output.

$$F = X + (Y' + Z) \cdot Z'$$

Circuit Diagram:

A	B	C	F

EXPERIMENT 4

Date Perform: _____

Boolean Expression Simplification with K Map**4.1 OBJECTIVES:**

- To become familiar with two standard forms of logic functions: SOP and POS.
- To become familiar that how a Boolean function can be minimized with the k-map and then can be expressed in gates

4.2 EQUIPMENT:

- Trainer Board
- 74XX quad 2-input gate IC
- Wires
- Wires Cutter
- IC Clipper

4.3 INTRODUCTION:

When a Boolean expression is implemented with logic gates, each term requires a gate, and each variable within the term designates an input to the gate. We define a literal as a single variable within the term that may or may not be complemented. By reducing the number of terms, the number of literals, or both in a Boolean expression, it is often possible to obtain a simpler circuit. Boolean algebra or K-map is applied to reduce an expression for the purpose of obtaining a simpler circuit. A Boolean function can be written in a variety of ways when expressed algebraically. There are, however, a few ways of writing algebraic expressions that are considered to be standard forms. The standard forms facilitate the simplification procedures for Boolean expressions and frequently result in more desirable logic circuits.

The standard forms contain product terms and sum terms. An example of a product term is XYZ. This is a logical product consisting of an AND operation among three literals. An example of a sum term is $X+Y+Z$. This is a logical sum consisting of OR operation among the literals.

In the sum of min-terms canonical form, every product term includes a literal of every variable of the function. Product terms of the SOP form which do not include a literal of a variable, say variable B, should be augmented by,

- AND-ing the product term which misses a literal of B with $(B + \bar{B})$
- Subsequently applying the distributive property to eliminate the parenthesis.

In the product of max-terms canonical form, every sum term includes a literal of every variable of the function. Sum terms of the POS form which do not include a literal of a variable, say variable B, ought to be augmented by,

- OR-ing the sum term with $B \cdot \bar{B}$
- Subsequently applying postulate $a+b \cdot c = (a+b) \cdot (a+c)$ to distribute the product $B \cdot \bar{B}$

Steps to Implement the Function:

1. Write the truth table for the function given above
2. Fill the k-map cells from the truth table
3. Simplify and minimize the function with k-map.
4. Write the simplified function from k-map.
5. Draw the circuit diagram and construct the circuit on the Trainer Board.

4.4LAB EXERCISE:

Task 1: Simplify following function using K map and implement simplified function

$$F(X, Y, Z) = \sum (1, 2, 4, 6, 7)$$

K-Map Simplification:

Simplified Expression:

F=

Circuit Diagram:

Draw the circuit diagram above mentioned function.

Task 2: Simplify following function using K map and implement simplified function

$$F(A, B, C, D) = \sum (2, 3, 6, 9, 10, 11, 14)$$

K-Map Simplification:

Simplified Expression:

F=

Circuit Diagram:

Draw the circuit diagram above mentioned function.

EXPERIMENT 5

Date Perform: _____

Universal Gates NAND/NOR Implementation

5.1 OBJECTIVES:

- To become familiar with the universal gates.
- To implement different logics using universal gates.

5.2 EQUIPMENT:

- Trainer Board
- Wires & Wires Cutter
- 7400 quad 2-input NAND gate IC
- 7402 quad 2-input NOR gate IC

5.3 INTRODUCTION:

Digital circuits are frequently constructed with NAND or NOR gates rather than with AND and OR gates. NAND and NOR gates are easier to fabricate with electronic components and are the basic gates used in all IC digital logic families. Because of the prominence of NAND and NOR gates in the design of digital circuits, rules and procedures have been developed for the conversion from Boolean functions given in terms of AND, OR, and NOT into equivalent NAND and NOR logic diagrams.

5.4 LAB TASKS

Task 1: XOR gate implementation using NAND Gate

XOR gate Boolean Function: $F =$

Step # 1: Draw and implement the given logic function with AND, OR and NOT gates

Step # 2: Replace AND, OR and NOT gates with equivalent NAND gate circuit

Step # 3: Simplify the circuit to get the final NAND equivalent circuit and implement using NAND gate.

Task 2: XNOR gate implementation using NOR Gate

XNOR gate Boolean Function: $F =$

Step # 1: Draw and Implement the given logic function with AND, OR and NOT gates.

Step # 2: Replace AND, OR and NOT gates with equivalent NOR gate circuit.

Step # 3: Simplify the circuit to get the final NOR equivalent circuit and implement using NOR gate.

EXPERIMENT 6

Date Perform: _____

Half Adder and Subtractor using Logic Gates**6.1 OBJECTIVES:**

- Design of Half Adder
- Design of Half Subtractor

6.2 EQUIPMENT:

- Trainer Board
- 74XX quad 2-input gate IC
- Wires
- Wires Cutter
- IC Clipper

6.3 INTRODUCTION:

In this lab, we will design arithmetic circuits that are combinational circuits. An arithmetic circuit performs arithmetic operations such as addition, multiplication, subtraction, and division with binary numbers or with decimal numbers in a binary code. Adder/subtractor is a very important component of digital system, ALU and Processor (CPU). A combinational circuit that performs the addition of two bits is called half adder. The circuit of half adder has two outputs, one sum(s) and other carry (c). For multi bit addition the carry obtained from the addition of two least significant bits is added to the next higher order pair of significant bits. A combinational circuit that performs the subtraction of two bits is called half subtractor. One that performs the subtraction of three bits (two significant bits and a previous borrow) is called full subtractor. The circuits of half subtractor have two outputs, one subtraction and other borrow.

6.4 PROCEDURE**(Half Adder and Half Subtractor):**

1. Connect the trainer with the power supply.
2. Install the ICs on the trainer board.
3. Wire according to the diagram.
4. Use the logic switches for input and connect output of Half Adder (Sum and Carry) and Subtractor (Difference and Bout) to the LEDs of trainer board.
5. Supply the VCC and GND to the pin 14 and 7 respectively.
6. Test all the possible combination of inputs and fill out the table.

Half Adder Truth Table:

Input		Output	
A	B	Sum	Carry

Boolean Functions of Output:

Sum =

Carry =

Circuit Diagram:

Draw the circuit diagram for Half adder using Boolean equations of Sum and Carry.

Half Subtractor Truth Table:

Input		Output	
A	B	diff	Borrow

Boolean Functions of Output:

Sum =

Carry =

Circuit Diagram:

Draw the circuit diagram and truth table of Half subtractor using Boolean equations of Difference and Borrow.

EXPERIMENT 7

Date Perform: _____

Two Bit Magnitude Comparator**7.1 OBJECTIVES:**

- To become familiar with the operation of Magnitude Comparator

7.2 EQUIPMENT REQUIRED:

- Trainer Board
- 74LS85 (4 Bit Magnitude Comparator)
- Basic Gates.
- Wires & Wire Cutter

7.3 INTRODUCTION:

The comparison of two numbers is an operation that determines if one number is greater than, equal to or less than the other number. A magnitude comparator is a combinational circuit that compares two numbers A and B and determines their relative magnitudes. The outcome of the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$, or $A < B$.

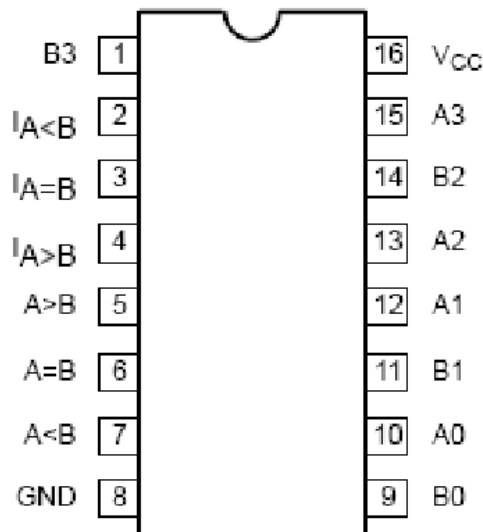
Pin Configuration of 74LS85:

Fig. 1: Pin Configuration of 74LS85.

7.4 LAB TASK:

1. Mount 4-bit magnitude comparator IC on trainer board.
2. Connect Pin 16 to 5V and Pin 8 to ground point
3. Connect toggle switches to the number inputs of IC.
4. Connect the IC output to the LED indicators on the trainer and observe the outputs.

Comparing Inputs				Outputs		
A3, B3	A2, B2	A1, B1	A0, B0	A>B	A=B	A<B
A3>B	X	X	X			
A3<B	X	X	X			
A3=B	A2>B2	X	X			
A3=B	A2<B2	X	X			
A3=B	A2=B2	A1>B1	X			
A3=B	A2=B2	A1<B1	X			
A3=B	A2=B2	A1=B1	A0>B0			
A3=B	A2=B2	A1=B1	A0<B0			
A3=B	A2=B2	A1=B1	A0=B0			

EXPERIMENT 8

Date Perform: _____

Decoder and Priority Encoder**8.1 OBJECTIVES:**

- Practicing the implementation of logic functions using MSI level functional blocks.
- Gaining experience with MSI level functional blocks/components whose outputs are active low.
- Gaining a close insight into the functioning and properties of encoder/decoder circuits
- Developing skills in the design and testing of combinational logic circuits.

8.2 EQUIPMENT:

- Trainer Board
- 74LS138 (3-to-8 Decoder)
- 74LS148 (8-bit Priority Binary Encoder)

8.3 INTRODUCTION:**Decoder**

Decoder is a multiple input, multiple output logic circuit that converts coded input into coded output, where the input and output codes are different. The input code generally has fewer bits than the output code, and there is one-to-one mapping, each input code word produces a different output code word. The most used input code is an n-bit binary code, where an n-bit word represents one of 2^n different coded values, i.e. n-to- 2^n decoder or binary decoder.

Encoder

Encoder is a logic circuit that has fewer output bits than the input code. The encoder takes 2^n inputs bits and generates n-bit output. Only one of the inputs can be 1, and the corresponding binary will display on the output bits. But when more than one input bits become 1 at the same time then what should be the output then? So we give priority to inputs and the input with high priority will freeze the output with its binary value. Such an encoder is called priority encoder.

Pin Configuration of 74LS138 (3-to-8 Decoder):

Proper value at the enable lines ($E_1 = 0$, $E_2 = 0$, $E_3 = 1$) will enable the decoder, all other combination of enable lines will keep the output lines high. These multiple enable lines are for building large decoders.

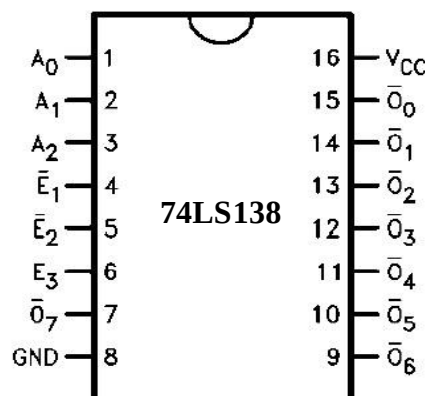


Fig 1: 3×8 Decoder IC

Circuit Diagram of 3-to-8 Decoder:

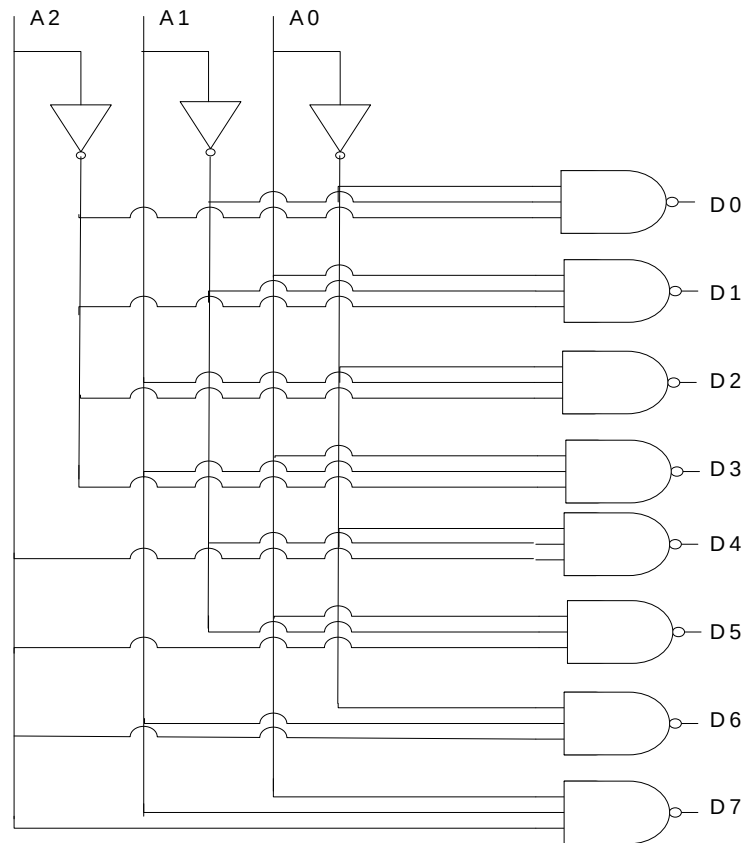


Fig 2: 3×8 Decoder Internal Structure

Outputs are active low. The binary value on A₂, A₁, A₀ will drive the corresponding output (D_i) to 0 all other will remain at 1.

INPUTS			OUTPUTS							
A ₀	A ₁	A ₂	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0								
1	0	0								
0	1	0								
1	1	0								
0	0	1								
1	0	1								
0	1	1								
1	1	1								

Pin Configuration of 74LS148 (8-to-3 Priority Encoder):

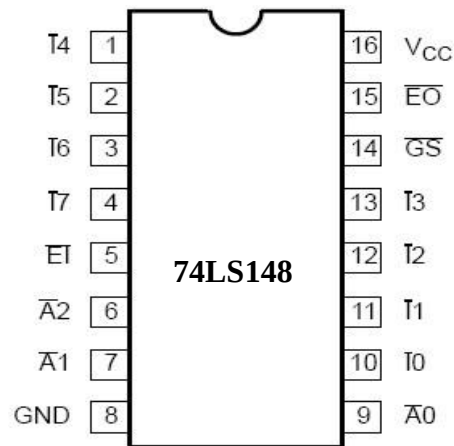


Fig 3: 8×3 Priority Encoder

Circuit Diagram of 8-to-3 Priority Encoder:

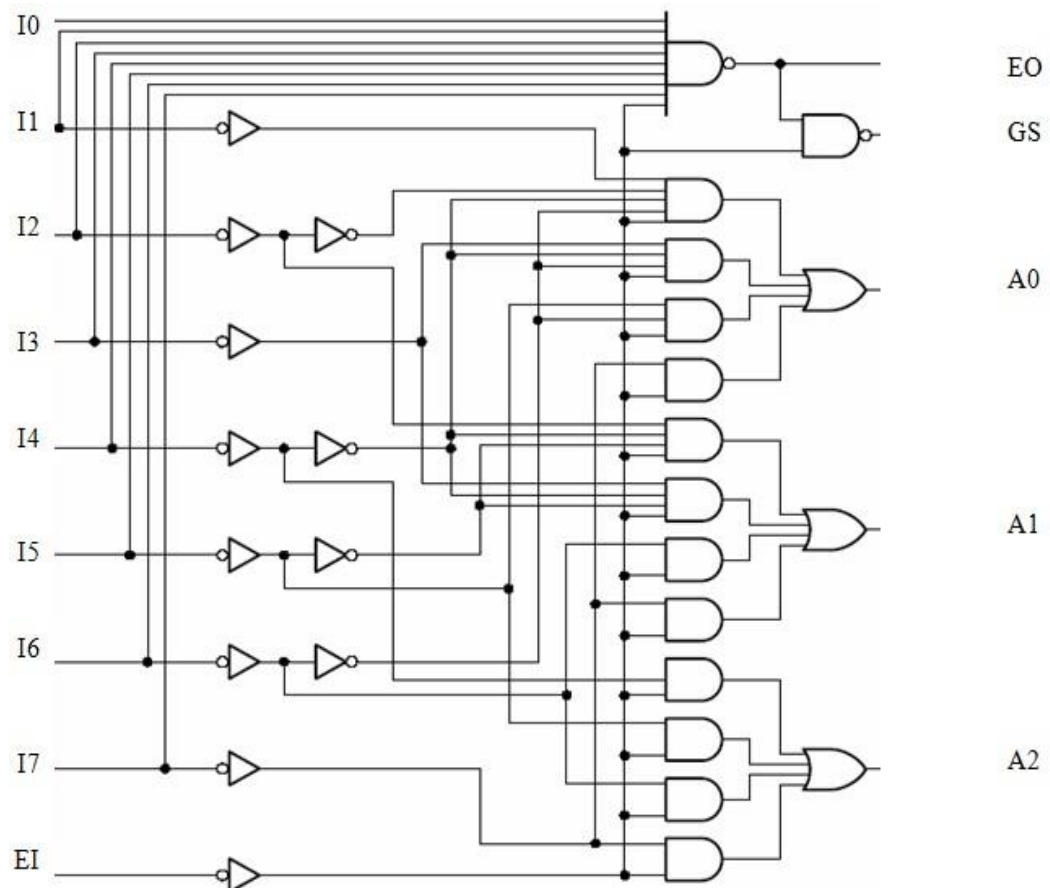


Fig 4: 8×3 Priority Encoder Internal Structure

Truth Table:

Inputs									Outputs				
EI	I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	GS	A ₂	A ₁	A ₀	EO
1	X	X	X	X	X	X	X	X					
0	1	1	1	1	1	1	1	1					
0	X	X	X	X	X	X	X	0					
0	X	X	X	X	X	X	0	1					
0	X	X	X	X	X	0	1	1					
0	X	X	X	X	0	1	1	1					
0	X	X	X	0	1	1	1	1					
0	X	X	0	1	1	1	1	1					
0	X	0	1	1	1	1	1	1					
0	0	1	1	1	1	1	1	1					

EXPERIMENT 9

Date Perform: _____

Multiplexer and De-multiplexer**9.1 OBJECTIVES:**

- To become familiar with the operation of MUX and De-MUX
- Practicing the implementation of logic functions using MSI level functional blocks
- Gaining a close insight into the functioning and properties of multiplexer (MUX) circuits.
- Practicing the implementation of logic functions using MSI level functional blocks.


9.2 EQUIPMENT:

- Trainer Board
- Bread Board
- 74LS138 (1-to-8 De-multiplexer)
- 74LS151 (8-to-1 Multiplexer)
- Wires
- Wires Cutter
- IC Clipper

9.3 INTRODUCTION:

A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs the information to a single output line. The selection of a input line is controlled by a set of input variables, called selection input. Normally, there are 2^n input lines and n selection inputs whose bit combination determines which input is selected.

A de-multiplexer is doing the opposite function of multiplexer. It takes input on a single input line and the select lines determines one of the 2^n output lines and the input contents is visible on that output.

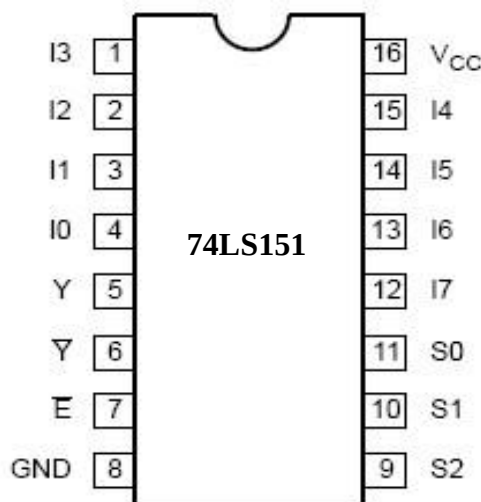Pin Configuration of 74LS151 (8 to 1 Mux):Fig 1: 8×1 Multiplexer IC

Circuit Diagram of 8×1 Multiplexer:

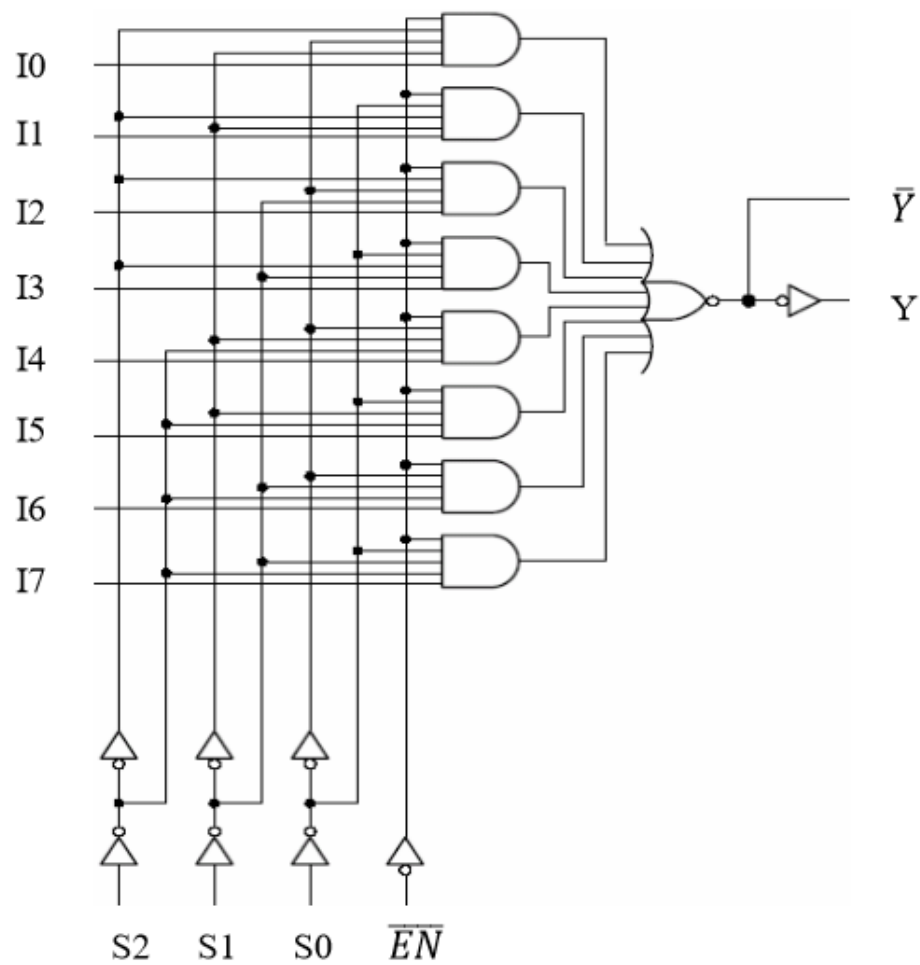


Fig 2: 8×1 Multiplexer Internal Structure

Truth Table:

Inputs				Outputs
E	S2	S1	S0	Y
1	X	X	X	
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	

Pin Configuration of 74LS138 (1×8 De multiplexer):

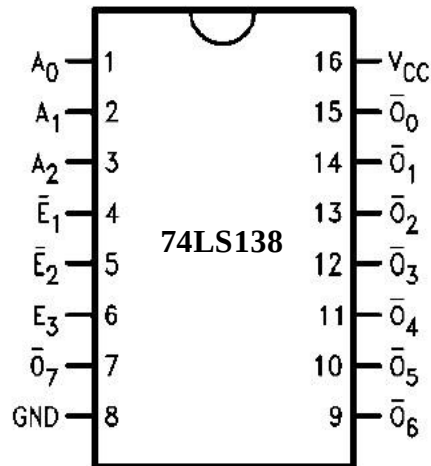


Fig 3: 1×8 DEMUX

Here any two of these should be hard wired i.e. $E_2 = 0$ and $E_3 = 1$, so the third enable pin (E_1) will act as input A_2 , A_1 , A_0 are acting as select lines of de-mux.

Circuit Diagram of 1-to-8 DEMUX:

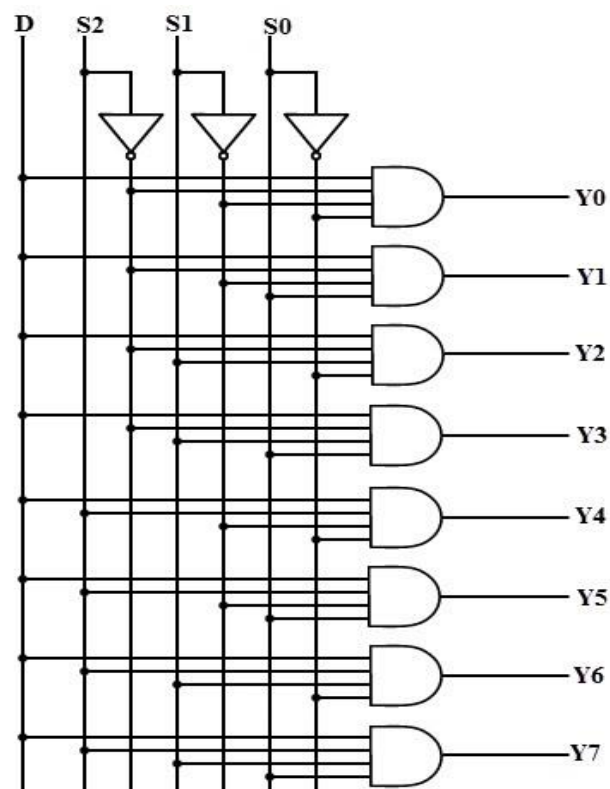


Fig 4: 8×1 DEMUX Internal Structure

Truth Table:

Inputs				Outputs							
D	S ₀	S ₁	S ₂	O ₀	O ₁	O ₂	O ₃	O ₄	O ₅	O ₆	O ₇
0	X	X	X								
1	0	0	0								
1	1	0	0								
1	0	1	0								
1	1	1	0								
1	0	0	1								
1	1	0	1								
1	0	1	1								
1	1	1	1								

EXPERIMENT 10

Date Perform: _____

7 segment Display & sequential Circuits**10.1 OBJECTIVES:**

- To become familiar with the operation of 7-segment display.
- Developing skills in the composition and testing of sequential logic circuits.
- Gaining a close insight into the functioning and properties of basic static memory circuits.

10.2 EQUIPMENT:

- Trainer Board
- 7448 BCD to 7-segment (common-cathode) decoder
- Common-cathode 7-segment LED Display
- 7400 NAND Gate IC
- 7474 Dual +ve edge triggered D-Flip Flop
- 74112 Dual -ve edge triggered JK-Flip Flop

10.3 INTRODUCTION:**7 segment Display:**

The numbers from 0 to 9 can be shown using a 7-segment LED display unit. This unit shows one decimal digit using 7 LED segments to form the numbers from 0 to 9. These 7-segments are a, b, c, d, e, f, g.

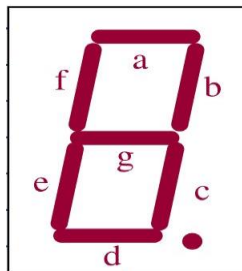


Figure 1: 7-Segment Display

The pin connections of the common-cathode and common anode 7-segment single digit display are below.

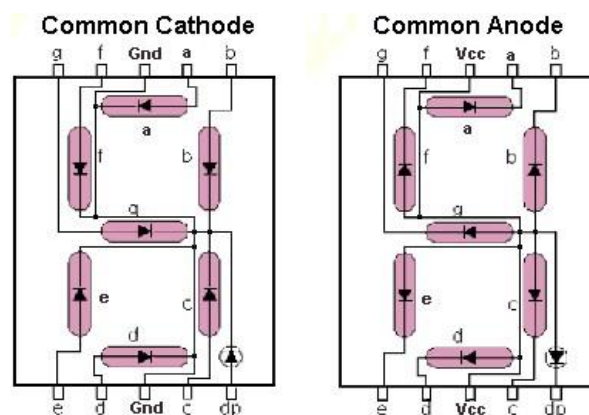


Figure 2: Common Cathode and Common Anode 7-segments

A 7448 chip can be used to construct the pattern of segments for each state of the counter's 4 lines or bits. Thus, the 7448 inputs are the 4 lines from the binary counter or from the input switches of Trainer board and its outputs are the 7 lines to the 7-segment LED Display showing the state of the segments. The 7448 is a BCD decoder so it only works for counter states between 0000 and 1001, i.e. decimal numbers 0 through 9.

Pin Configuration of 74LS48(BCD to 7-Segment Decoder):

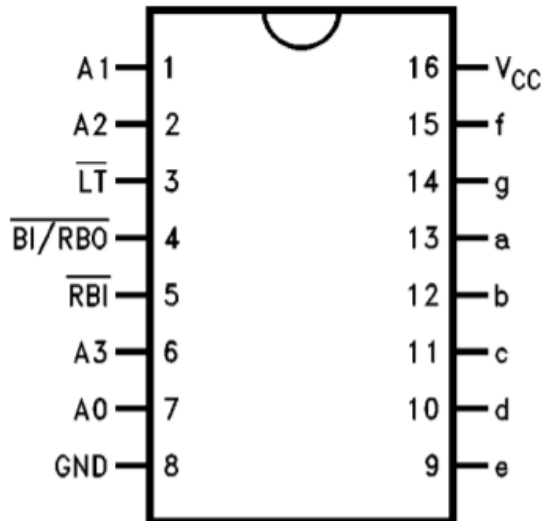


Figure 3: BCD to 7-Segment Decoder

Sequential Circuit:

A sequential circuit consists of a combinational circuit to which storage elements are connected to form a feedback path. The storage elements are devices capable of storing binary information. The binary information stored in these elements at any given time defines the state of the sequential circuit at that time. There are two main types of sequential circuits: Synchronous sequential circuit and Asynchronous sequential circuit.

Latches and Flip Flops:

Latches and Flip Flops are used to store binary information in sequential circuits. Storage element can maintain a binary state indefinitely if power is delivered to the circuit. The major differences among various types of storage elements are in the number of inputs they possess and in the way the inputs affect the binary state. Storage element that operates with signal levels (rather than signal transitions) are referred to as latch and those controlled by a clock transition are flip-flops. Latches are said to be level sensitive devices; flip-flops are edge-sensitive devices. The two types of storage elements are related because latches are the basic circuits from which all flip-flops are constructed by latches.

Latches and Flip Flops have different operating modes. For Latches, operating modes are “**SET MODE, RESET MODE, NO CHANGE MODE, FORBIDDEN MODE**”. In case of Flip Flops, operating modes are “**SET MODE, RESET MODE, NO CHANGE MODE, COMPLEMENT MODE**”.

“**NO CHANGE MODE**” sometimes is considered as “**MEMORY MODE**”.

Pin Configuration of 74112 (JK-FFP):

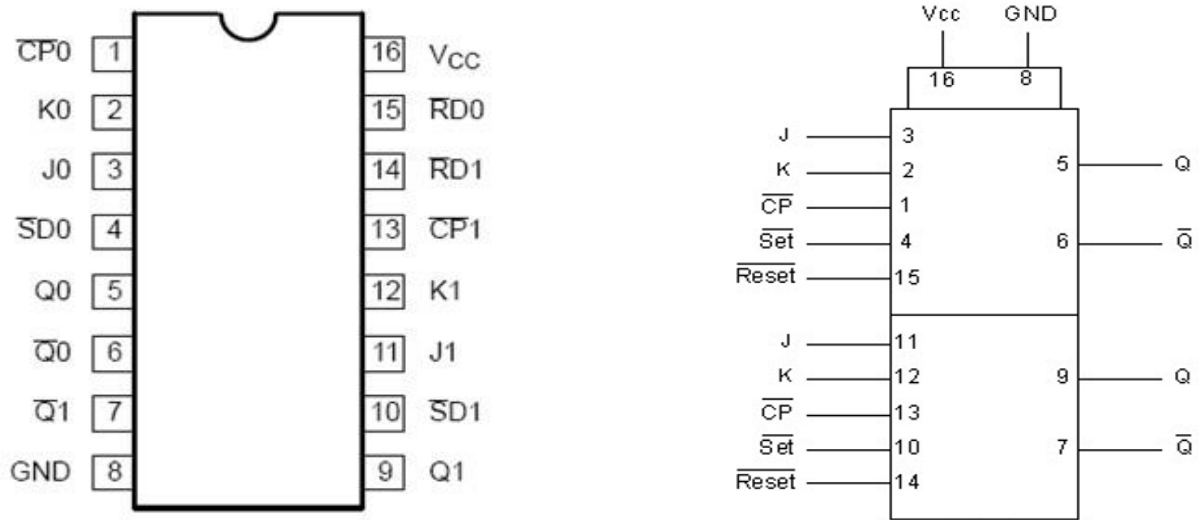


Figure 4: Dual JK-Flip Flop IC & Logic Symbol

Pin Configuration of 7474 (D-FFP):

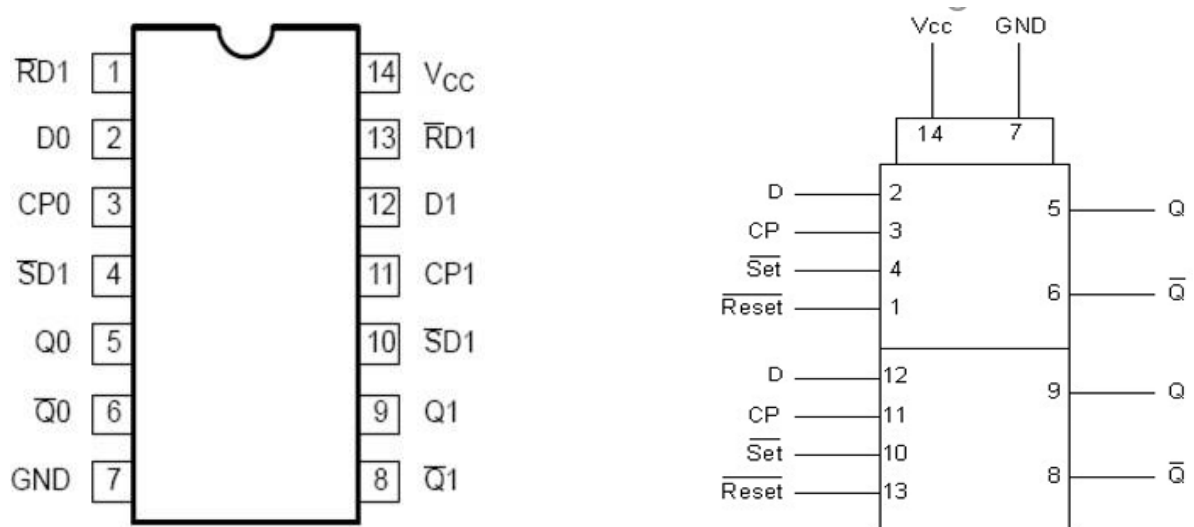


Figure 5: Dual D-Flip Flop IC & Logic Symbol

Task 1:

Connect Common-cathode 7-segment LED Display with 7448 BCD to 7-segment and show different digits. Also connect BCD display and show Hexadecimal digits.

Task 2:

Construct a SR latch using NAND Gates and fill the given table.

--	--

Table 10.1: SR-Latch Function Table

S	R	Q	Q'	MODE OF OPERATION
0	1			
1	1			
1	0			
0	0			

Task 3:

Connect a JK Flip Flop IC and Record observations and given table.

Inputs					Outputs		Operating Mode
SD	RD	CP	J	K	Q	Q'	
0	1	X	X	X			
1	0	X	X	X			
0	0	X	X	X			
1	1	↓	1	1			
1	1	↓	0	1			
1	1	↓	1	0			
1	1	↓	0	0			
1	1	1	X	X			

Task 4:

Connect D Flip Flop IC and Record observations in following Table.

Inputs				Outputs		Operating Mode
SD	RD	CP	D	Q	Q'	
0	1	X	X			
1	0	X	X			
0	0	X	X			
1	1	↑	1			
1	1	↑	0			
1	1	1	X			

EXPERIMENT 11

Date Perform: _____

Universal Shift Register**11.1 OBJECTIVES:**

- Getting familiar with the design of sequential circuits on the register transfer level.
- Gaining a close insight into the functioning and properties of the universal shift register.
- Developing skills in the composition and testing of sequential logic circuits.

11.2 EQUIPMENT:

- Trainer Board
- 74194 4-bit Universal Shift Register
- Function Generator

11.3 INTRODUCTION:**Registers:**

A register is used to store n-bits of information, where n is number of flip-flops. A register consists of a set of flip-flops, together with gates that perform data processing tasks. The flip-flops hold data, and the gates determine the new or transformed data to be transferred into the flip-flops. The registers have two types, one simple register and other register with parallel load. The register with parallel load is the register in which we can easily store the value of our own choice. This ability of register is controlled by a control input, if control input is 1 then the data which we want to enter is stored on the register, and when the value is 0 then the data which was stored in the register remain stored in the register.

Shift Registers:

Another type of register is known as shift register. The shift register is capable of shifting its stored bits laterally in one or both direction. The logical configuration of a shift register consists of a chain of flip-flops in cascade, with the output of one flip-flop connected to the input of the next flip flop. All flip-flops receive a common clock pulse, which activates the shift from each stage to the next.

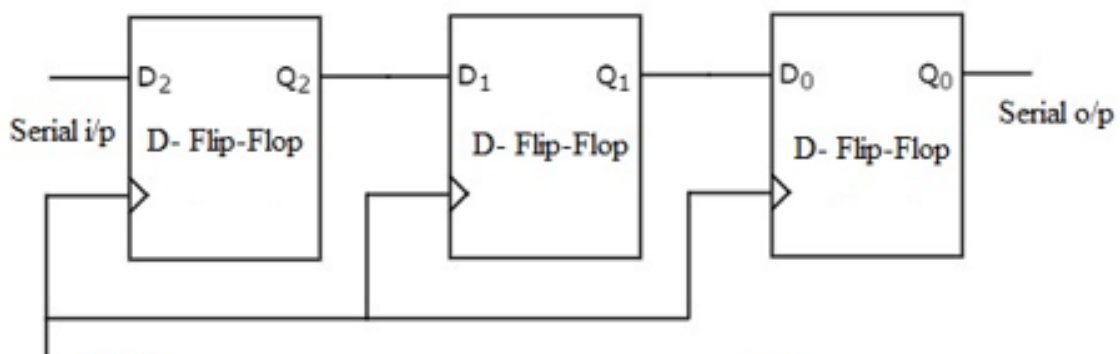


Figure 1: Shift Register

Circuit Diagram for 4-bit shift register:

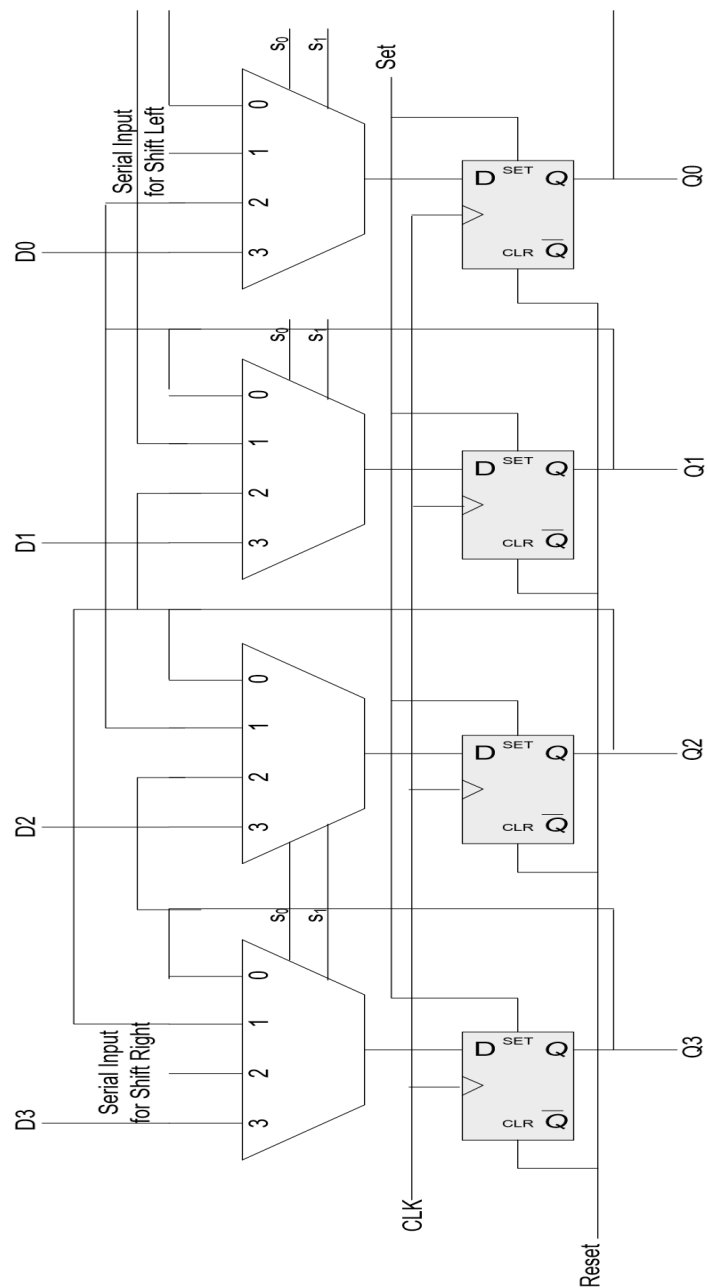


Figure 2: 4-bit Shift Register Internal Structure

Pin Configuration of 74LS194:

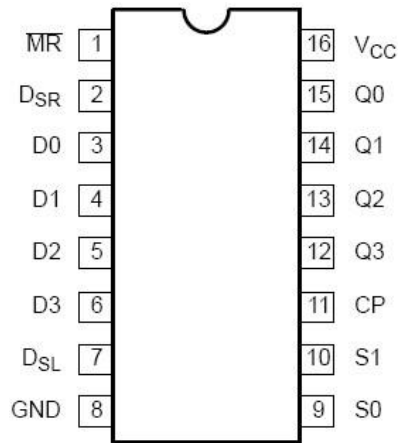


Figure 3: 4-bit Shift Register IC

The shift register is to be operated according to the following function table.

Mode Selection		Register Operations
S_1	S_0	
0	0	No Change
0	1	Shift Right
1	0	Shift Left
1	1	Parallel Load Data

Table 1: 4-bit Universal Shift Register Mode Selection

Procedure:

- Connect the trainer with the power supply
- For clock, connect function generator with the power supply. Keep frequency knob on minimum, press the button for function of square wave and keep the frequency range on minimum, rotate the amplitude knob to max and get the output from it. Connect the red alligator clip with the CP pin of the IC and ground the black alligator clip.
- Mount the IC 74LS194 on the trainer board
- Supply the VCC and GND to the pin 16 and 8 respectively
- Wire the pins of IC, refer to the pin configuration.
- Drive the D's, Dsr, Dsl, S0 & S1 inputs with input switches on the trainer board and CP input from the clock on the trainer board. Connect output Q's to LEDs.
- Connect the Master Reset (MR) to input switch. When low will reset the register.
- Apply different combinations on S1, S0 and verify the corresponding function.
- Observe and record the output on the LEDs.

Task:

Connect 4-bit Shift Register IC and verify the operations of Shift Register.

EXPERIMENT 12

Date Perform: _____

Counters**12.1 OBJECTIVES:**

- To become familiar with the operation of Dual 4-bit Counter IC 74393.
- To understand the difference between Synchronous and Asynchronous Counters.
- To become familiar with the State Excitation Table.
- To develop skills of constructing Counters with JK Flip Flops.

12.2 EQUIPMENT:

- Trainer Board.
- 7 segment BCD Display.
- 74XX gate ICs.
- 74112 –ve edge triggered JK-Flip Flop.
- Dual 4-bit Counter IC 74393.

12.3 INTRODUCTION:

A register that goes through a prescribed sequence of states upon the application of input pulses is called a counter. The input pulses may be clock pulses or may originate from some other source, and they may occur at fixed intervals of time or random intervals. The sequence of states may follow the binary number sequence or any other sequence of states: A counter that follows the binary number sequence is called a binary counter.

Counters are available in two categories: **ripple counters and synchronous counters**. In a ripple counter, the flip-flop output transition serves as a source for triggering other flip-flops. In other words, the clock inputs of some or all the flip-flops are triggered not by the common clock pulses, but rather by the transition that occurs in other flip-flop outputs. In a synchronous counter, the clock inputs of all of the flip-flops receive the common clock pulse, and the change of state is determined from the present state of the counter.

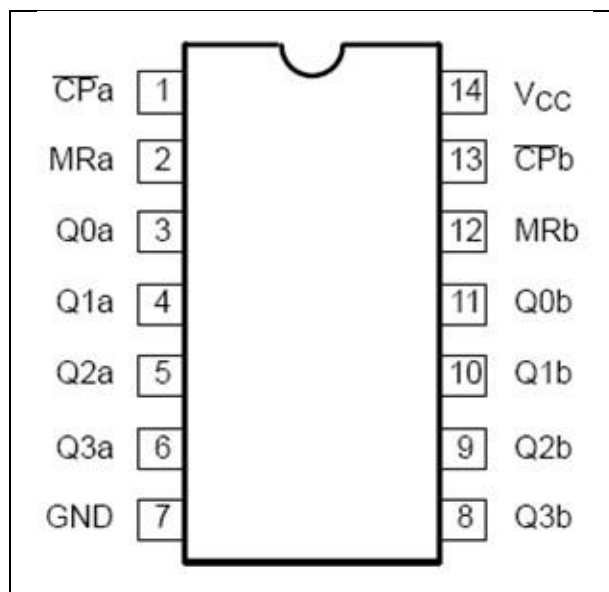
Pin Configuration of 74393:

Figure 1: Dual 4-bit Synchronous Counter

Pin Configuration of 74112 (JK-FFP):

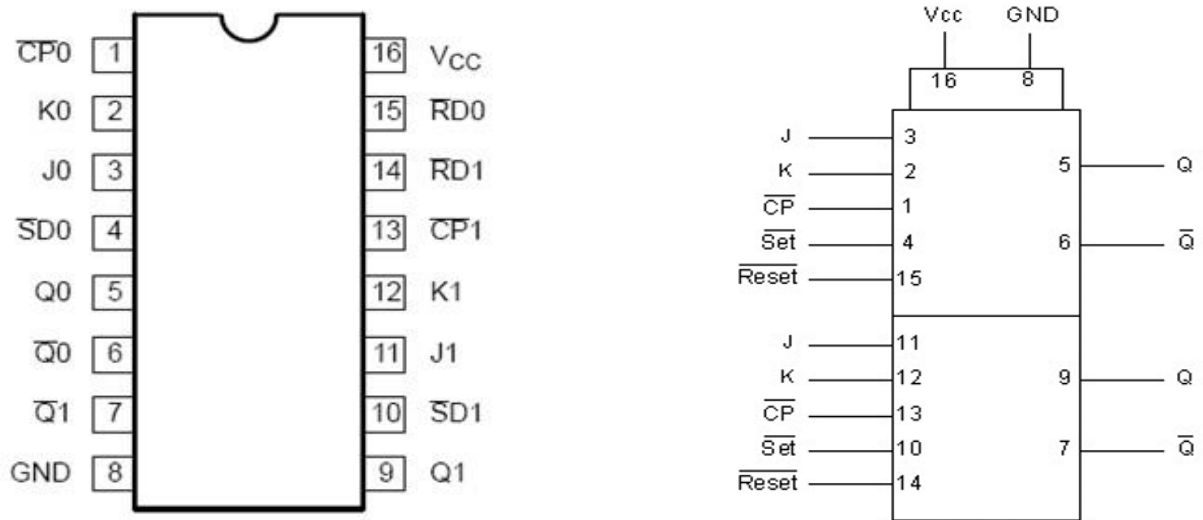



Figure 2: Dual JK-Flip Flop IC & Logic Symbol

Procedure:

- Connect the trainer with the power supply.
- For clock, connect function generator with the power supply. Keep frequency knob on minimum, press the button for function of square wave and keep the frequency range on minimum, rotate the amplitude knob to max and get the output from it.
- Connect the red wire with the CP pin of the IC and ground the Black pin.
- Mount the ICs on the trainer board.
- Supply the V_{CC} and GND to the respective pins.
- Wire the pins of IC according to the diagram, refer to the pin configuration of ICs.
- Drive Up/Down with the input switch on the trainer board and CP input from the clock on the trainer board. Connect output Q's to LEDs
- Connect reset input to the switch. When high will reset the counter.
- Observe and record the output on the LEDs

Task 1: Construct 3-bit ripple/asynchronous up counter using JK flipflop.

Circuit Diagram

 

Draw state diagram



Task 2: Construct 3-bit synchronous up counter using JK flipflop (Attach Handwritten Solutions of your Design).

1. How many Flip Flops are required?

2. Fill the excitation table of J K Flip Flop

Qn	Qn+1	J	K

3. Draw excitation table of the circuit.

4. K-map simplification of circuit

5. Draw circuit diagram of your design

A large, empty rectangular box with a thin black border, intended for the student to draw their circuit diagram. It occupies the majority of the page below the instruction.

Appendix A: Lab Evaluation Criteria

Labs with Project/Case Study/With Open Ended lab:

1. Labs	50%
2. Open Ended Lab	10%
3. Project (Design Project) or Case Study	20%
<i>Project:</i>	
a. Project Hardware or Software Implementation	40% to 60%
b. Project Report/ Viva	40% to 60%
<i>Case Study:</i>	
a. Case Study Report	60% to 70%
b. Presentation	30% to 40%
4. Final Exam	20%
Total	100%

Labs with Project/Case Study/Without Open Ended lab:

1. Labs	60%
2. Project (Design Project) or Case Study	20%
<i>Project:</i>	
a. Project Hardware or Software Implementation	40% to 60%
b. Project Report/ Viva	40% to 60%
<i>Case Study:</i>	
a. Case Study Report	60% to 70%
b. Presentation	30% to 40%
3. Final Exam	20%
Total	100%

Notice:

Copying and plagiarism of lab manuals is a serious academic misconduct. First instance of copying may entail ZERO in that experiment. Second instance of copying may be reported to DC. This may result in awarding FAIL in the lab course.

Appendix B: Safety around Electricity

In all the Electrical Engineering (EE) labs, with an aim to prevent any unforeseen accidents during conduct of lab experiments, following preventive measures and safe practices shall be adopted:

- Remember that the voltage of the electricity and the available electrical current in EE labs has enough power to cause death/injury by electrocution. It is around 50V/10 mA that the “cannot let go” level is reached. “The key to survival is to decrease our exposure to energized circuits.”
- If a person touches an energized bare wire or faulty equipment while grounded, electricity will instantly pass through the body to the ground, causing a harmful, potentially fatal, shock.
- Each circuit must be protected by a fuse or circuit breaker that will blow or “trip” when its safe carrying capacity is surpassed. If a fuse blows or circuit breaker trips repeatedly while in normal use (not overloaded), check for shorts and other faults in the line or devices. Do not resume use until the trouble is fixed.
- It is hazardous to overload electrical circuits by using extension cords and multi-plug outlets. Use extension cords only when necessary and make sure they are heavy enough for the job. Avoid creating an “octopus” by inserting several plugs into a multi-plug outlet connected to a single wall outlet. Extension cords should ONLY be used on a temporary basis in situations where fixed wiring is not feasible.
- Dimmed lights, reduced output from heaters and poor monitor pictures are all symptoms of an overloaded circuit. Keep the total load at any one time safely below maximum capacity.
- If wires are exposed, they may cause a shock to a person who comes into contact with them. Cords should not be hung on nails, run over or wrapped around objects, knotted or twisted. This may break the wire or insulation. Short circuits are usually caused by bare wires touching due to breakdown of insulation. Electrical tape or any other kind of tape is not adequate for insulation!
- Electrical cords should be examined visually before use for external defects such as: Fraying (worn out) and exposed wiring, loose parts, deformed or missing parts, damage to outer jacket or insulation, evidence of internal damage such as pinched or crushed outer jacket. If any defects are found the electric cords should be removed from service immediately.
- Pull the plug not the cord. Pulling the cord could break a wire, causing a short circuit.
- Plug your heavy current consuming or any other large appliances into an outlet that is not shared with other appliances. Do not tamper with fuses as this is a potential fire hazard. Do not overload circuits as this may cause the wires to heat and ignite insulation or other combustibles.
- Keep lab equipment properly cleaned and maintained.
- Ensure lamps are free from contact with flammable material. Always use lights bulbs with the recommended wattage for your lamp and equipment.
- Be aware of the odor of burning plastic or wire.
- ALWAYS follow the manufacturer recommendations when using or installing new lab equipment. Wiring installations should always be made by a licensed electrician or other qualified person. All electrical lab equipment should have the label of a testing laboratory.
- Be aware of missing ground prong and outlet cover, pinched wires, damaged casings on electrical outlets.

Lab Manual of 'Digital Logic Design'

- Inform Lab engineer / Lab assistant of any failure of safety preventive measures and safe practices as soon you notice it. Be alert and proceed with caution at all times in the laboratory.
- Conduct yourself in a responsible manner at all times in the EE Labs.
- Follow all written and verbal instructions carefully. If you do not understand a direction or part of a procedure, ASK YOUR LAB ENGINEER / LAB ASSISTANT BEFORE PROCEEDING WITH THE ACTIVITY.
- Never work alone in the laboratory. No student may work in EE Labs without the presence of the Lab engineer / Lab assistant.
- Perform only those experiments authorized by your teacher. Carefully follow all instructions, both written and oral. Unauthorized experiments are not allowed.
- Be prepared for your work in the EE Labs. Read all procedures thoroughly before entering the laboratory. Never fool around in the laboratory. Horseplay, practical jokes, and pranks are dangerous and prohibited.
- Always work in a well-ventilated area.
- Observe good housekeeping practices. Work areas should be kept clean and tidy at all times.
- Experiments must be personally monitored at all times. Do not wander around the room, distract other students, startle other students or interfere with the laboratory experiments of others.
- Dress properly during a laboratory activity. Long hair, dangling jewelry, and loose or baggy clothing are a hazard in the laboratory. Long hair must be tied back, and dangling jewelry and baggy clothing must be secured. Shoes must completely cover the foot.
- Know the locations and operating procedures of all safety equipment including fire extinguisher. Know what to do if there is a fire during a lab period; "Turn off equipment, if possible and exit EE lab immediately."